
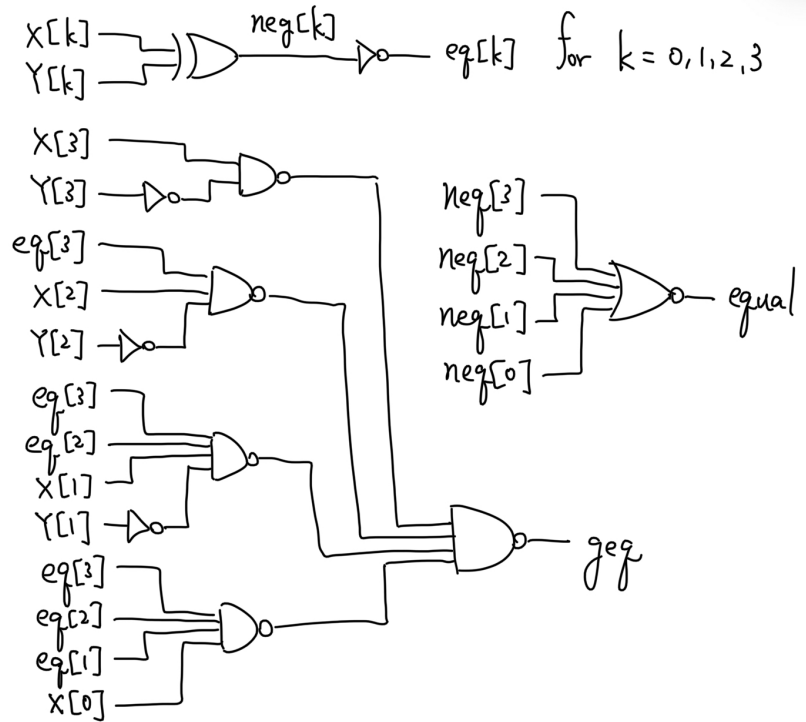


IC Design Homework 3



B07502028 吳宗翰

1. Circuit Diagram.


(1) CMP4

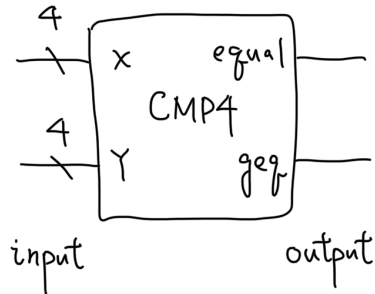

(2) MUX4

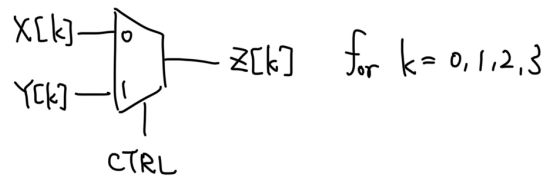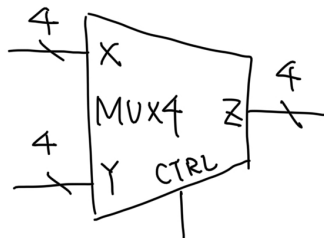


(3) Pairwise compare the five inputs.

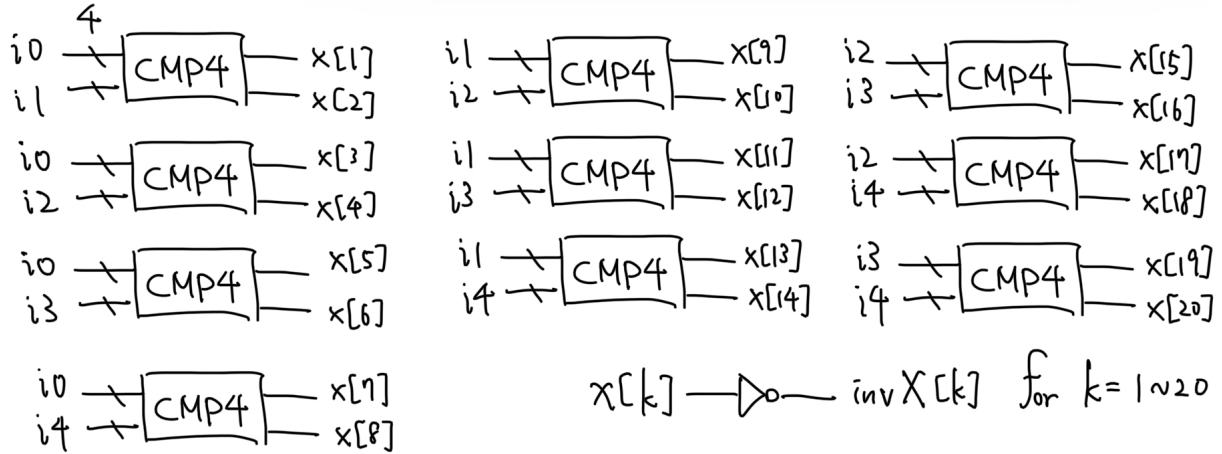



$x[1] = 1$	$i_0 = i_1$	$x[11] = 1$	$i_1 = i_3$
$x[2] = 1$	$i_0 \geq i_1$	$x[12] = 1$	$i_1 \geq i_3$
$x[3] = 1$	$i_0 = i_2$	$x[13] = 1$	$i_1 = i_4$
$x[4] = 1$	$i_0 \geq i_2$	$x[14] = 1$	$i_1 \geq i_4$
$x[5] = 1$	$i_0 = i_3$	$x[15] = 1$	$i_2 = i_3$
$x[6] = 1$	$i_0 \geq i_3$	$x[16] = 1$	$i_2 \geq i_3$
$x[7] = 1$	$i_0 = i_4$	$x[17] = 1$	$i_2 = i_4$
$x[8] = 1$	$i_0 \geq i_4$	$x[18] = 1$	$i_2 \geq i_4$
$x[9] = 1$	$i_1 = i_2$	$x[19] = 1$	$i_3 = i_4$
$x[10] = 1$	$i_1 \geq i_2$	$x[20] = 1$	$i_3 \geq i_4$

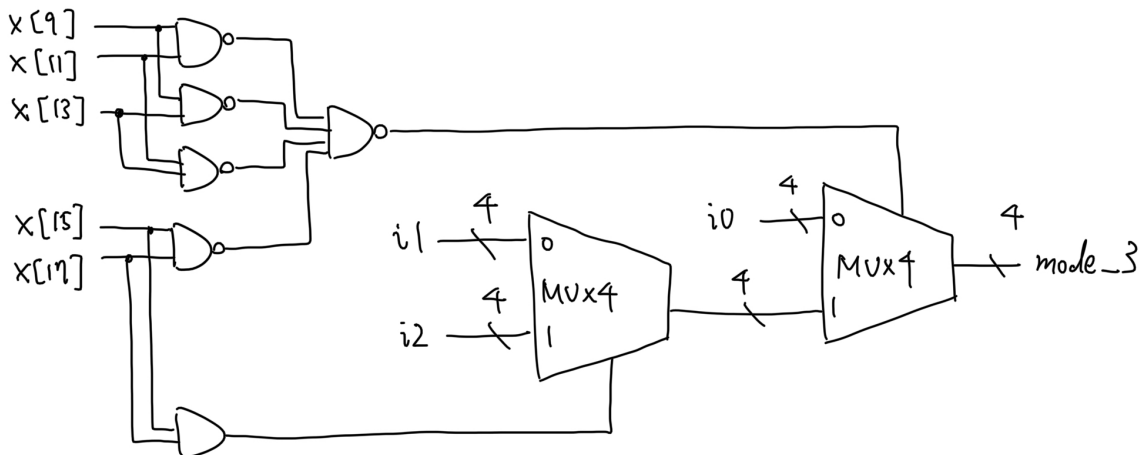(4) Case i: more than three inputs are the same
(e.g. 3,4,5,3,3; 0,2,2,0,2; 14,14,5,14,14; 1,1,1,1,1)




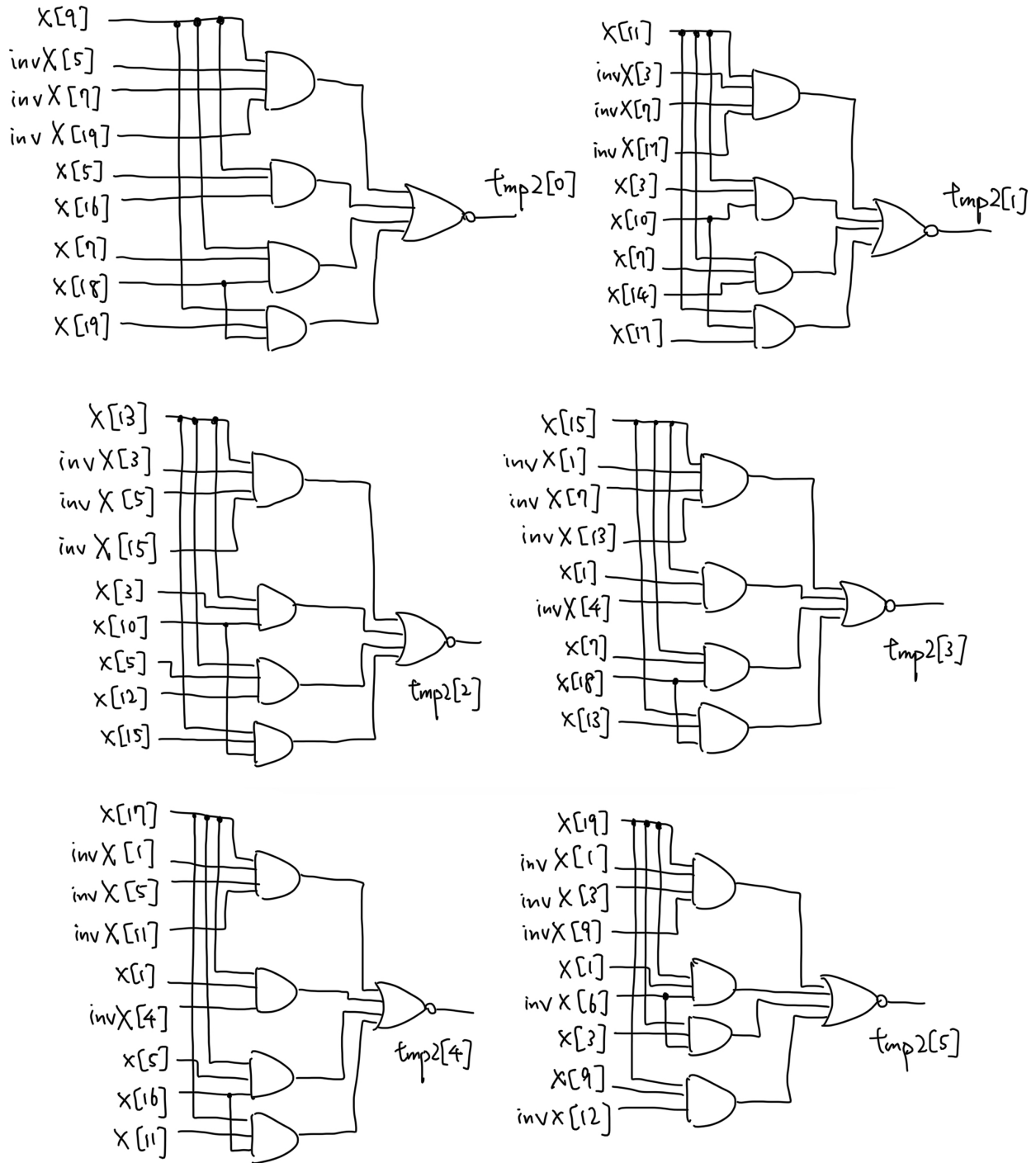(5) Case ii: two but no more than three inputs are the same (e.g. 3,7,14,14,4; 10,10,1,1,7)




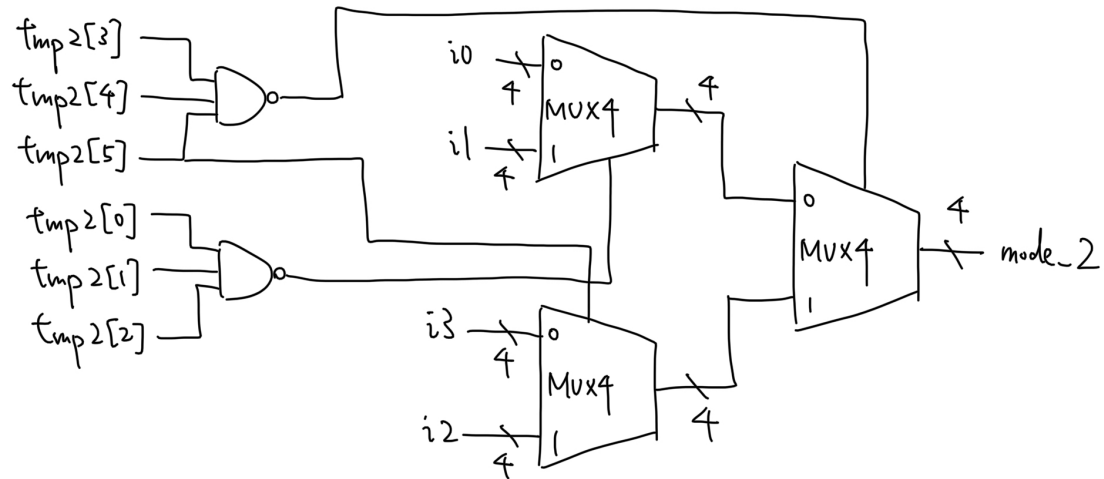

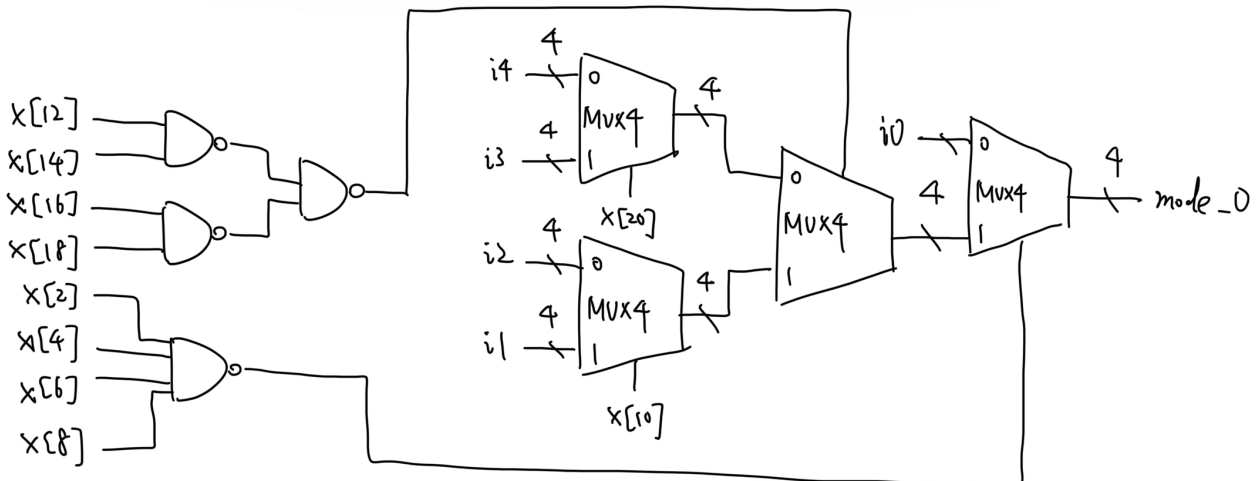
(6) Case iii: all five inputs are different (e.g. 10,5,4,7,3; 9;2;3;15;0)



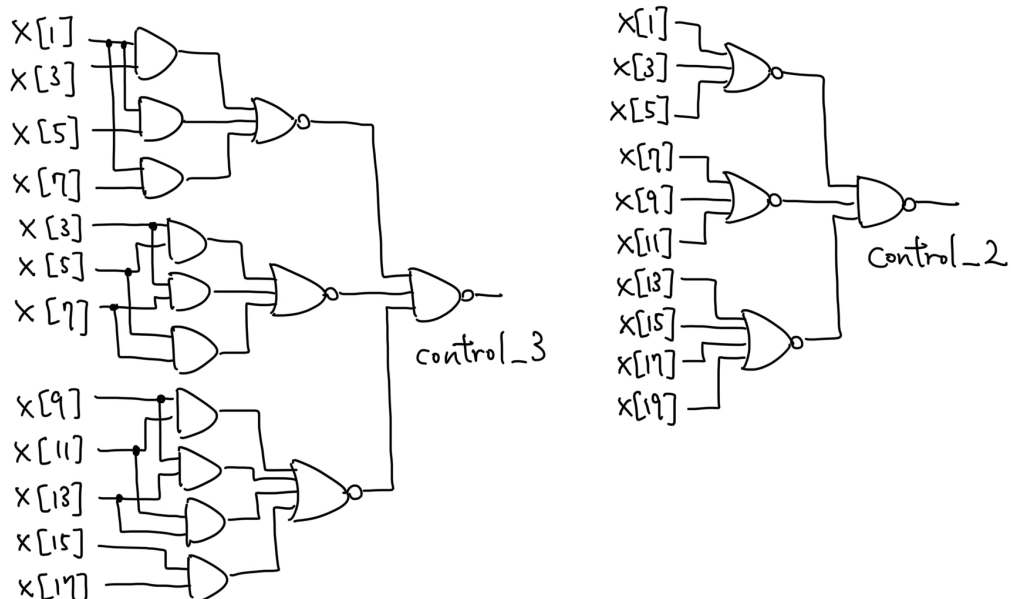(7) Generate control signals to determine which result (case i, ii or iii) should be the output.



(8) Output the result.

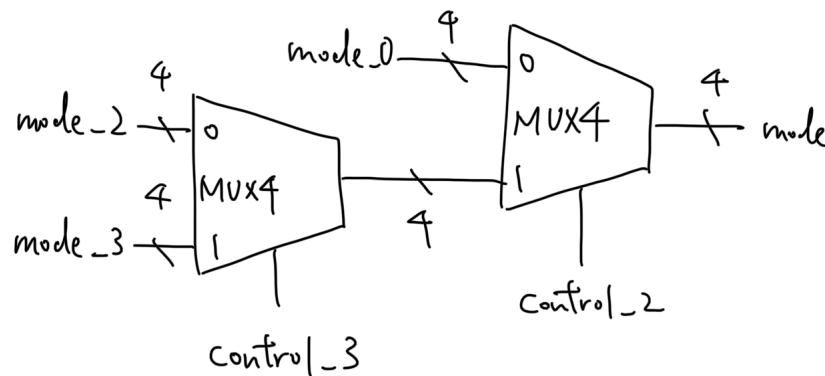

2. Discussion.

There are three cases:

- i. At least three inputs are identical.

If no more than three inputs among i_1 , i_2 , i_3 , i_4 are identical, output i_0 .

If i_2 , i_3 , i_4 are the same, output i_2 .

In all other situations, output i_1 .

- ii. Two but no more than three inputs are identical.

The condition for a pair of numbers to be the mode is that they have the same value, and other three numbers are different from one another, or there is a pair among the other three numbers but they are smaller. For example, the condition for i_3 , i_4 to be the mode is: $(i_3 = i_4 \text{ and } i_0 \neq i_1 \text{ and } i_0 \neq i_2 \text{ and } i_1 \neq i_2)$ or $(i_3 = i_4 \text{ and } i_0 = i_1 \text{ and } i_3 > i_0)$ or $(i_3 = i_4 \text{ and } i_0 = i_2 \text{ and } i_3 > i_2)$ or $(i_3 = i_4 \text{ and } i_1 = i_2 \text{ and } i_3 > i_1)$.

- iii. All five inputs are different numbers. Just choose the largest input. For example, the condition for i_1 to be the mode is: $i_1 > i_0 \text{ and } i_1 > i_2 \text{ and } i_1 > i_3 \text{ and } i_1 > i_4$.

When an input combination comes, calculate the output values for these three cases based on the logic circuit, and then use control signals (`control_2` and `control_3`) to determine which case happens and output the corresponding result. If we don't handle these three cases separately, the control signals for multiplexers (for determining which of the five input numbers appears at output) are becoming more complex, hence leading to more stages of logic gates and lengthening the critical path.